EXERCISE 01

1. Draw the schematic diagram for the following figure

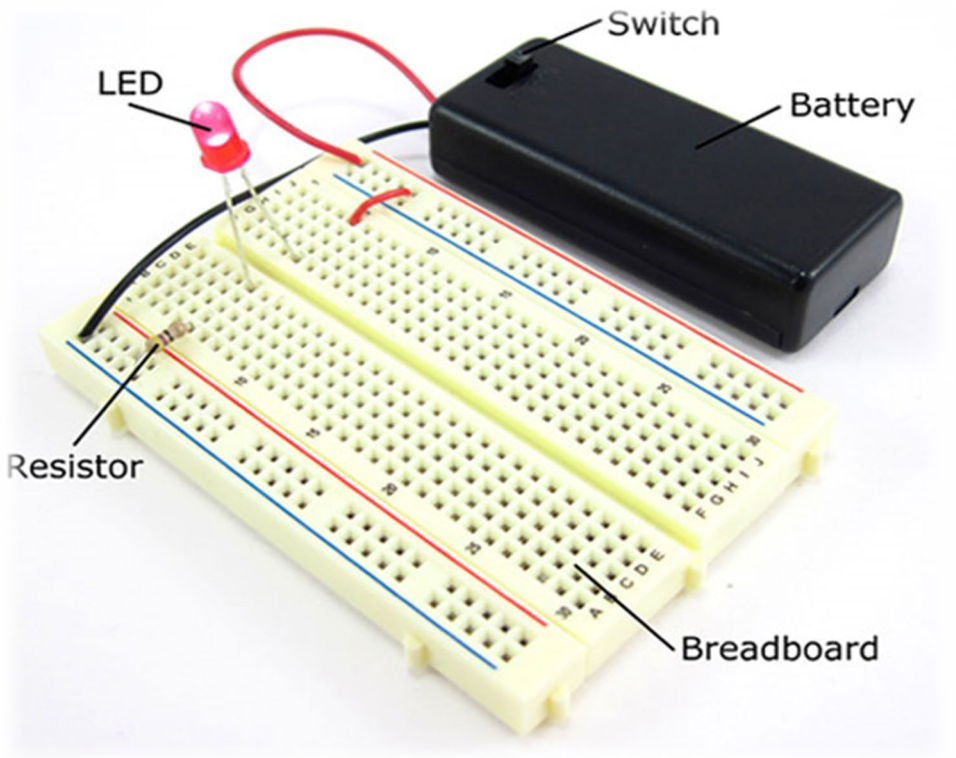

EXERCISE 01

Exercise 01: Answer

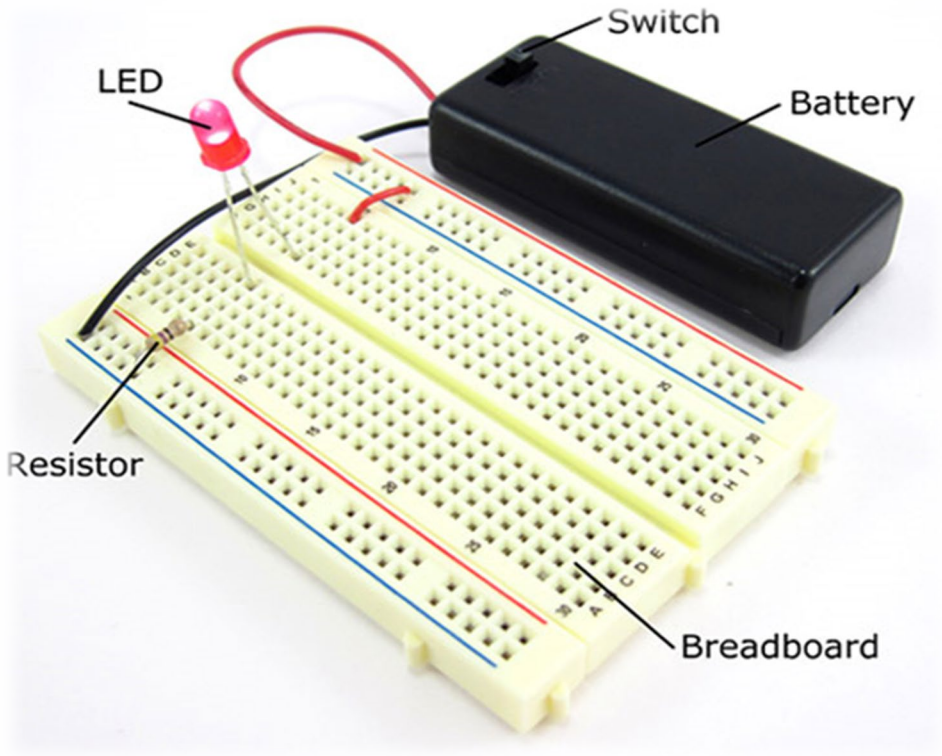

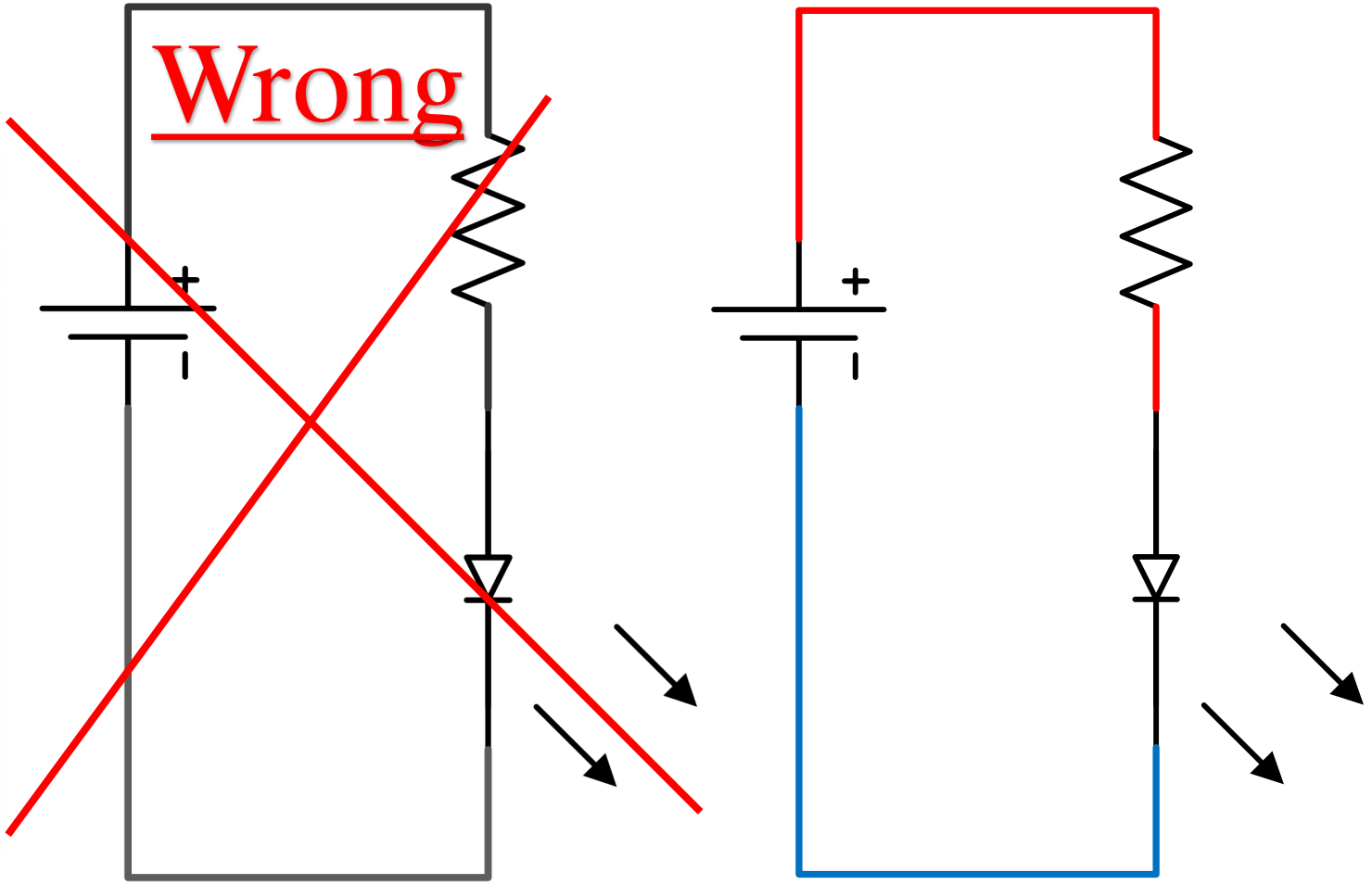

EXERCISE 2

How will you connect the circuit diagram by using a bread board?

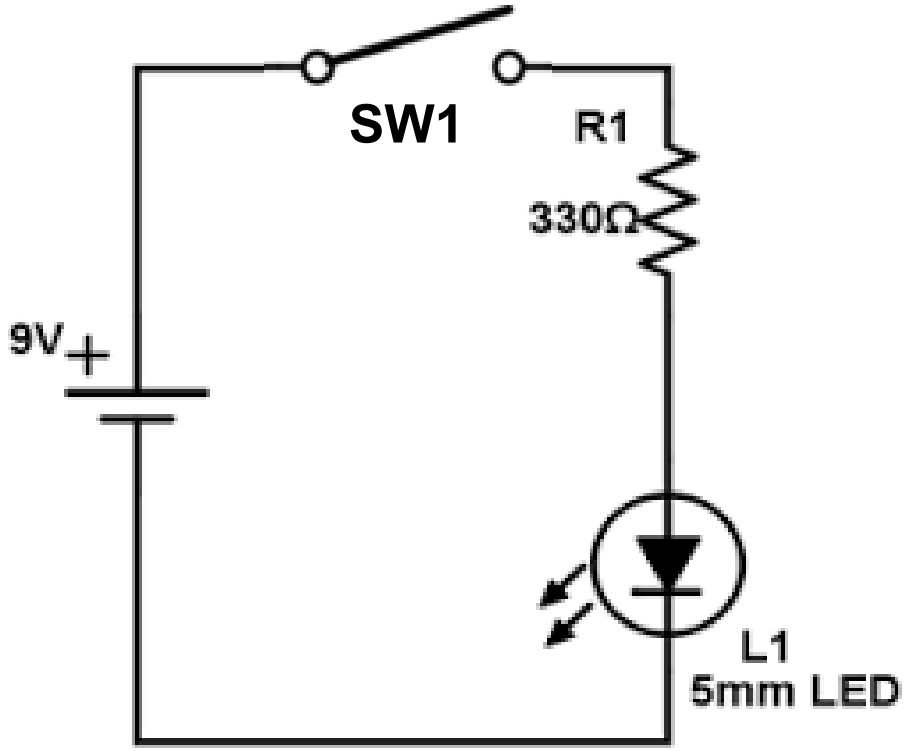

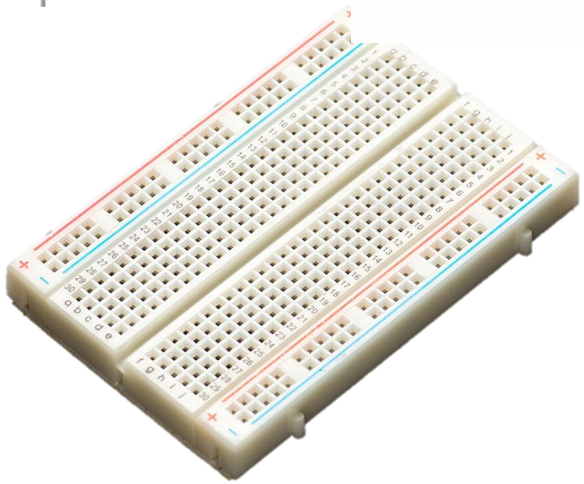

EXERCISE 2

Exercise 2: Answer

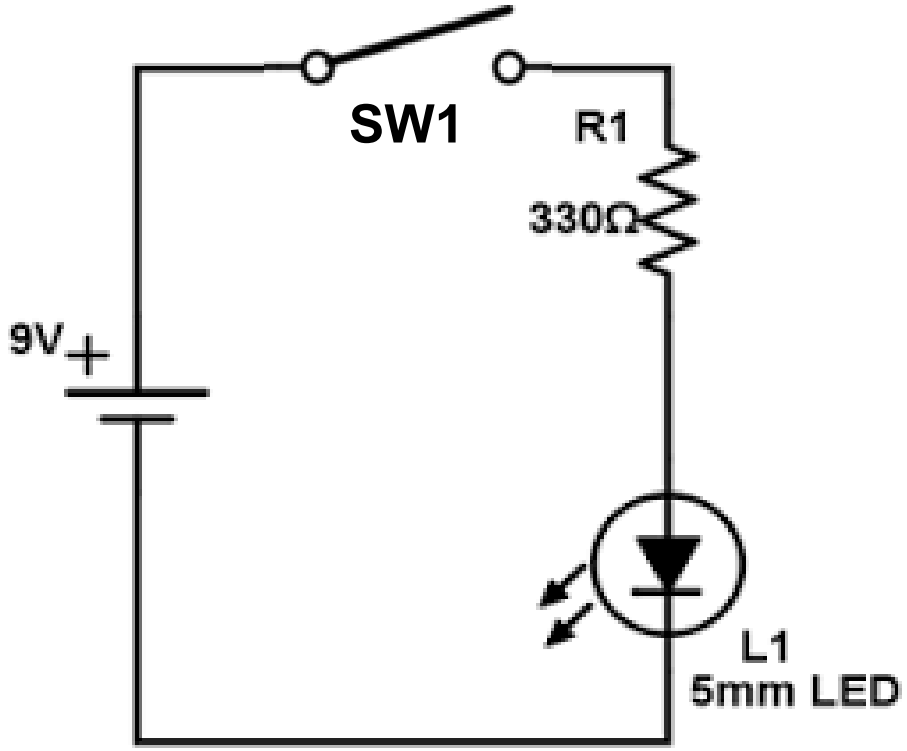

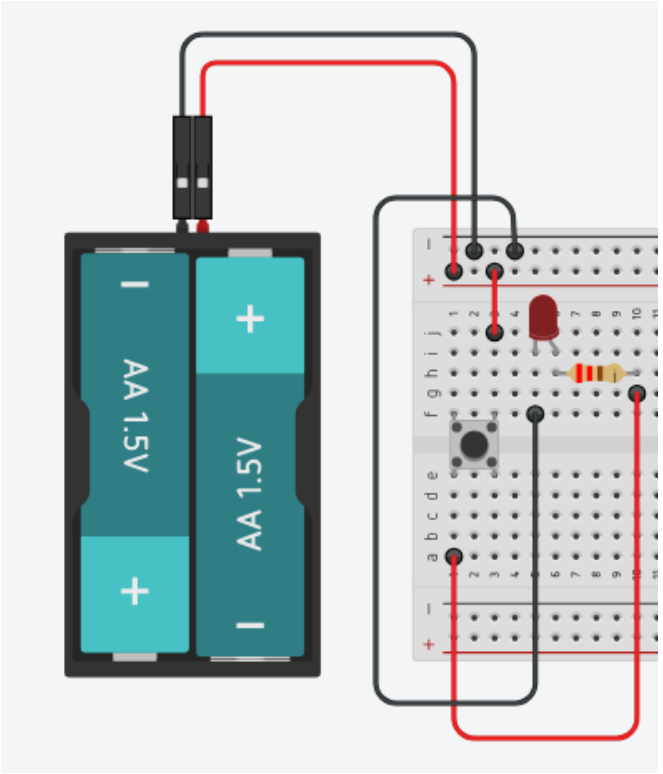

EXERCISE 3

How will you connect the circuit diagram by using a bread board?

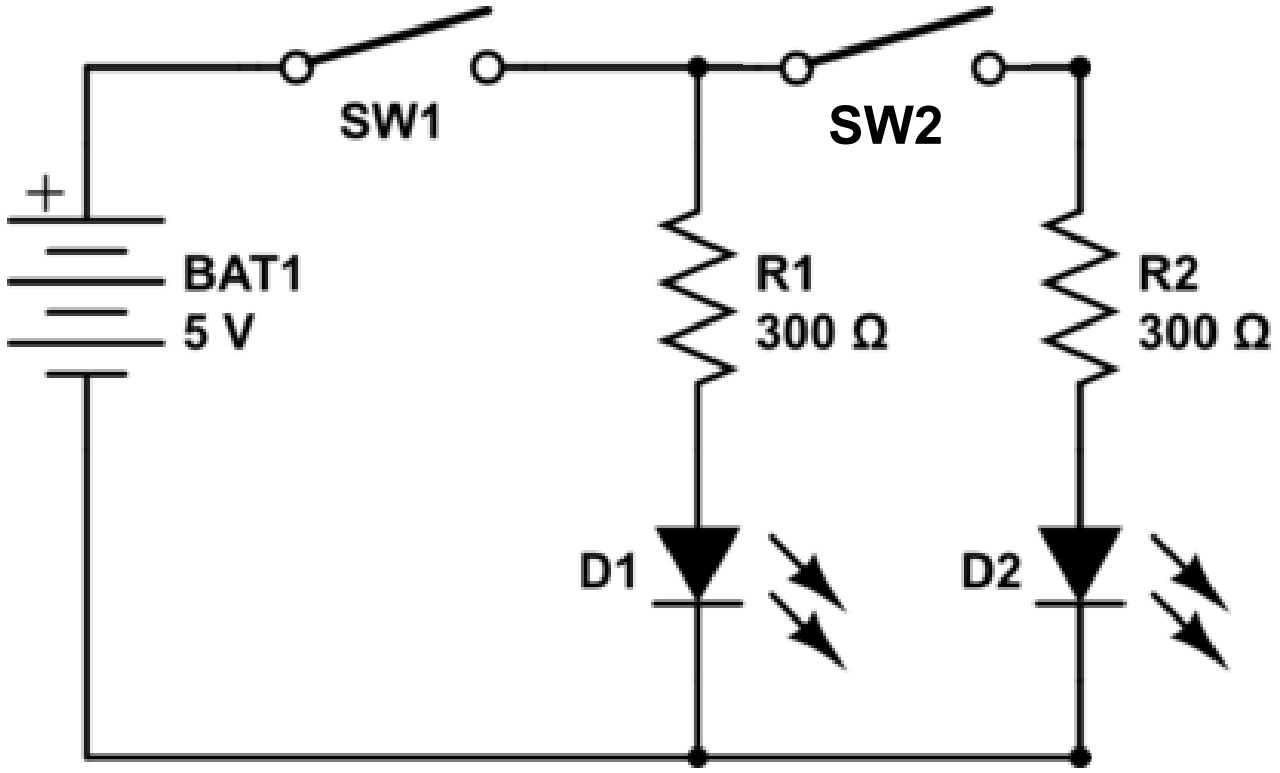

EXERCISE 3

Exercise 3 : Answer